



การจัดองค์การคอมพิวเตอร์

Arithmetic Logic Unit

31110321 Computer Organization

สำหรับนักศึกษาชั้นปีที่ 3 สาขาวิชาวิศวกรรมคอมพิวเตอร์

ทรงฤทธิ์ กิติศรีวรพันธุ์


songrit@npu.ac.th

สาขาวิชาวิศวกรรมคอมพิวเตอร์
มหาวิทยาลัยนครพนม

Outline

- 2.1 เลขไบนารี
- 2.2 การบวกเลขไบนารี
- 2.3 ตัวเลขลบ ในระบบดิจิทัล
- **2.4 Arithmetic Logic Unit (ALU)**
- 2.5 โปรเจกต์สปีดดาห์ (พฤษภัตถ์)
- 2.6 ภาพรวม


Von Neumann Architecture

 

- 1945 John Von Neumann
- เสนอสถาปัตยกรรมคอมพิวเตอร์สำหรับ
- ใช้งานได้หลากหลาย


ส่วนประมวลผลคณิตศาสตร์

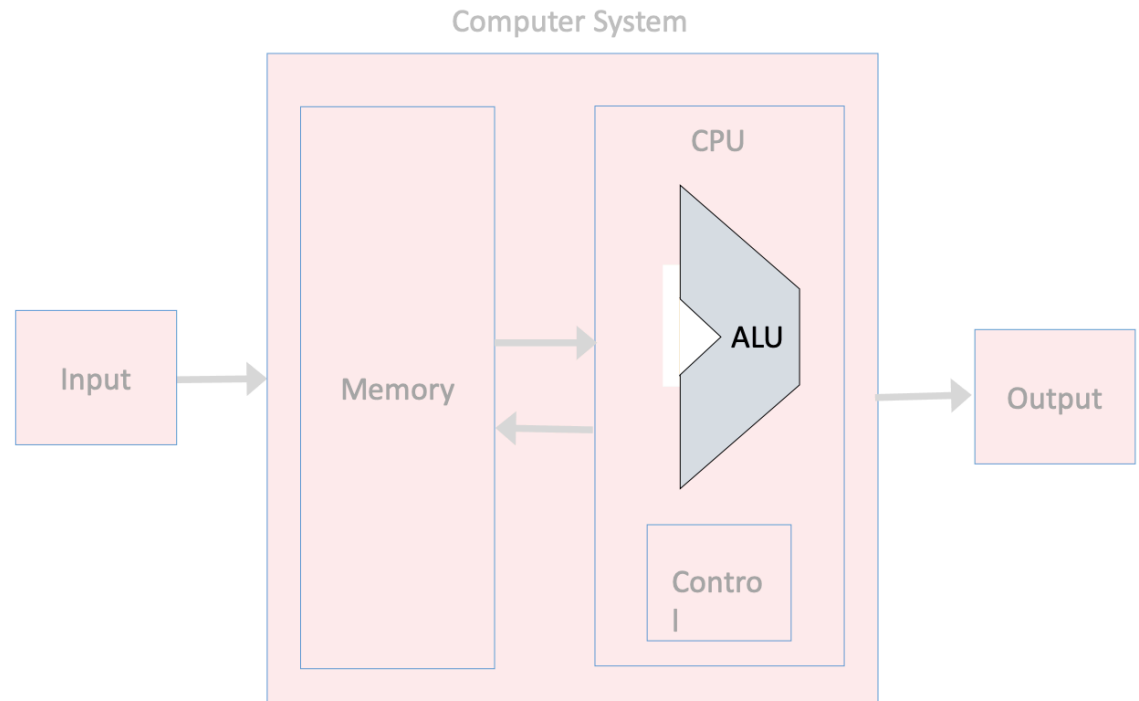- อุปกรณ์สำคัญ ของสถาปัตยกรรมฟอนนอยด์มัน คือ
- ส่วนประมวลผลคณิตศาสตร์
- หรือ เอแอลยู (ALU)




Arithmetic Logical Unit

 - ส่วนคำนวณเลขไบนารี มีการรับข้อมูล 2 ชุด เพื่อนำข้อมูลนั้นมาประมวลผลกัน
- ป้อนคำสั่งประมวลผลที่ตำแหน่ง f
 - บวก
 - ลบ
 - เลื่อนบิต และ อื่น
- เมื่อคำนวณเสร็จส่งออก
 - $F(\text{input1}, \text{input2})$




Hack ALU

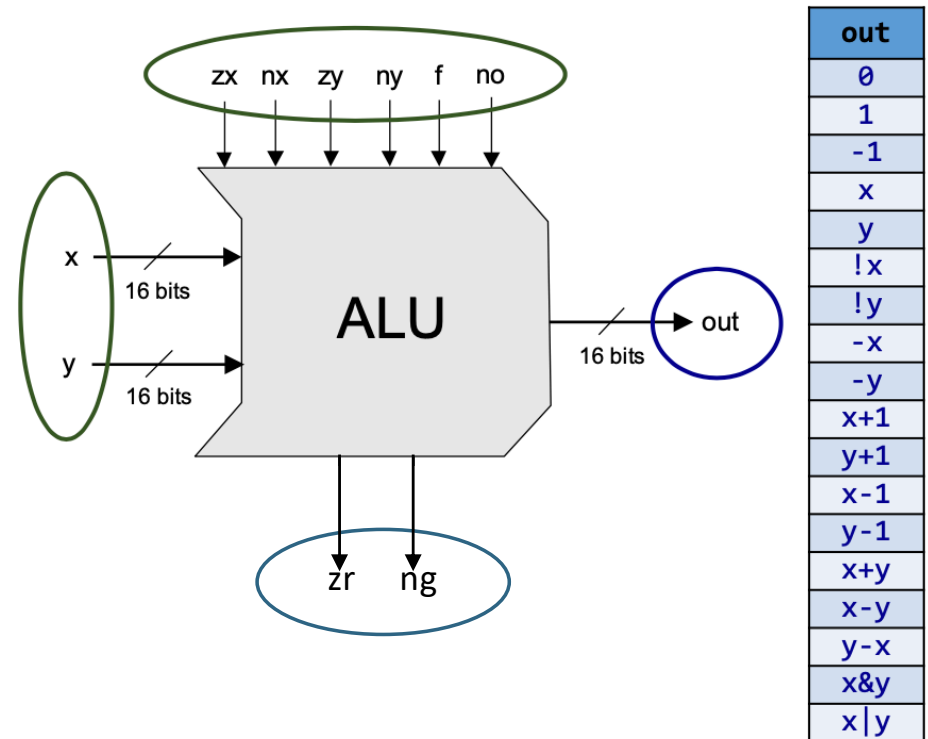- คำนวณครั้งละ 16-bit
- คำนวณเลขลบ แบบ two's complement
- บัสอินพุต 16บิต 2 บัส
- มีคำสั่ง 6 บิต
- ส่งออกบัสเอาต์พุต 16บิต
- มี 2 บิตเอาต์พุต (zr, ng)



Control Bit

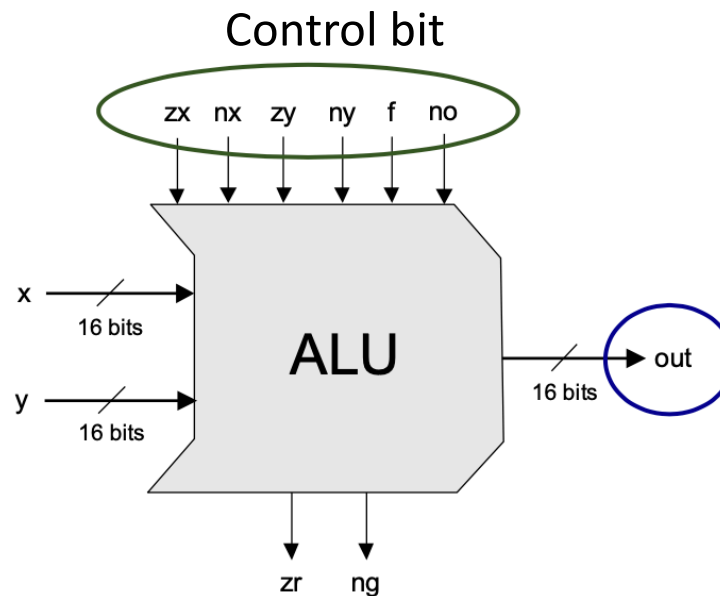- ALU ทำงานด้วยการ
ส่งคำสั่งใน Control
Bit
- เราได้ออกแบบคำสั่ง
Control bit เป็น
ตามตาราง



Control bit						
zx	nx	zy	ny	f	no	out
1	0	1	0	1	0	0
1	1	1	1	1	1	1
1	1	1	0	1	0	-1
0	0	1	1	0	0	x
1	1	0	0	0	0	y
0	0	1	1	0	1	!x
1	1	0	0	0	1	!y
0	0	1	1	1	1	-x
1	1	0	0	1	1	-y
0	1	1	1	1	1	x+1
1	1	0	1	1	1	y+1
0	0	1	1	1	0	x-1
1	1	0	0	1	0	y-1
0	0	0	0	1	0	x+y
0	1	0	0	1	1	x-y
0	0	0	1	1	1	y-x
0	0	0	0	0	0	x&y
0	1	0	1	0	1	x y

Hack ALU : คำนวณ $y-x$

The screenshot shows the Hack ALU GUI with several annotations:

- Load tools/builtInChips/ALU.hdl**: Points to the file selection button in the top toolbar.
- 2. Evaluate the chip logic**: Points to the 'Evaluate' button in the top toolbar.
- 1. Set the ALU's inputs and control bits to some test values (000111 codes "output y-x")**: Points to the control bits input field, which is set to 000111.
- 3. Inspect the ALU outputs**: Points to the output display, which shows -10, 0, and 1.
- Built-in ALU implementation**: Points to the HDL code window.
- The built-in ALU implementation has some GUI side-effects**: Points to the ALU chip icon in the bottom right.

The HDL code window contains the following text:

```
HDL
// This file is part of the material for
// "The Elements of Computing Systems"
// MIT Press. Book site: www.northeastern.edu/elements
// File name: tools/builtIn/ALU.hdl

/**
 * The ALU. Computes a pre-defined operation
 * where x and y are two 16-bit integers
 * by a set of 6 control bits described below.
 * The ALU operation can be described as follows:
 * * if zx=1 set x = 0
 * * if nx=1 set x = !x
 * * if zy=1 set y = 0
 * * if ny=1 set y = !y
 */
```

The ALU chip icon in the bottom right shows the following values:


- D Input : 30
- M/A Input : 20
- ALU output : -10

Hack ALU : คำนวณ $x \& y$

The screenshot shows the Hack ALU simulator interface. The top menu bar includes File, View, Run, and Help. Below the menu is a toolbar with icons for running, stepping, and other functions. The main window is divided into several sections:


- Input pins:** A table showing the values of input pins. The values for `x[16]` and `y[16]` are circled in green. The values for `zx`, `nx`, `zy`, `ny`, `f`, and `no` are all 0.
- Output pins:** A table showing the values of output pins. The value for `out[16]` is circled in blue. The values for `zr` and `ng` are 0.
- HDL:** A text area showing the HDL code for the ALU. The code is commented out, showing the logic for computing `x & y`.
- Annotations:** Three orange callout boxes provide instructions:
 - "Set the ALU's inputs and control bits to some test values (000000 codes 'compute x&y')"
 - "Inspect the ALU outputs"
 - "Set to binary I/O format"
- ALU Diagram:** A small diagram at the bottom right shows the ALU block with inputs `D Input` (-5242) and `M/A Input` (6253), and output `ALU output` (2052).

Hack ALU black box

 


The Hack ALU operation

zx	nx	zy	ny	f	no	out
if zx then x=0	if nx then x=!x					

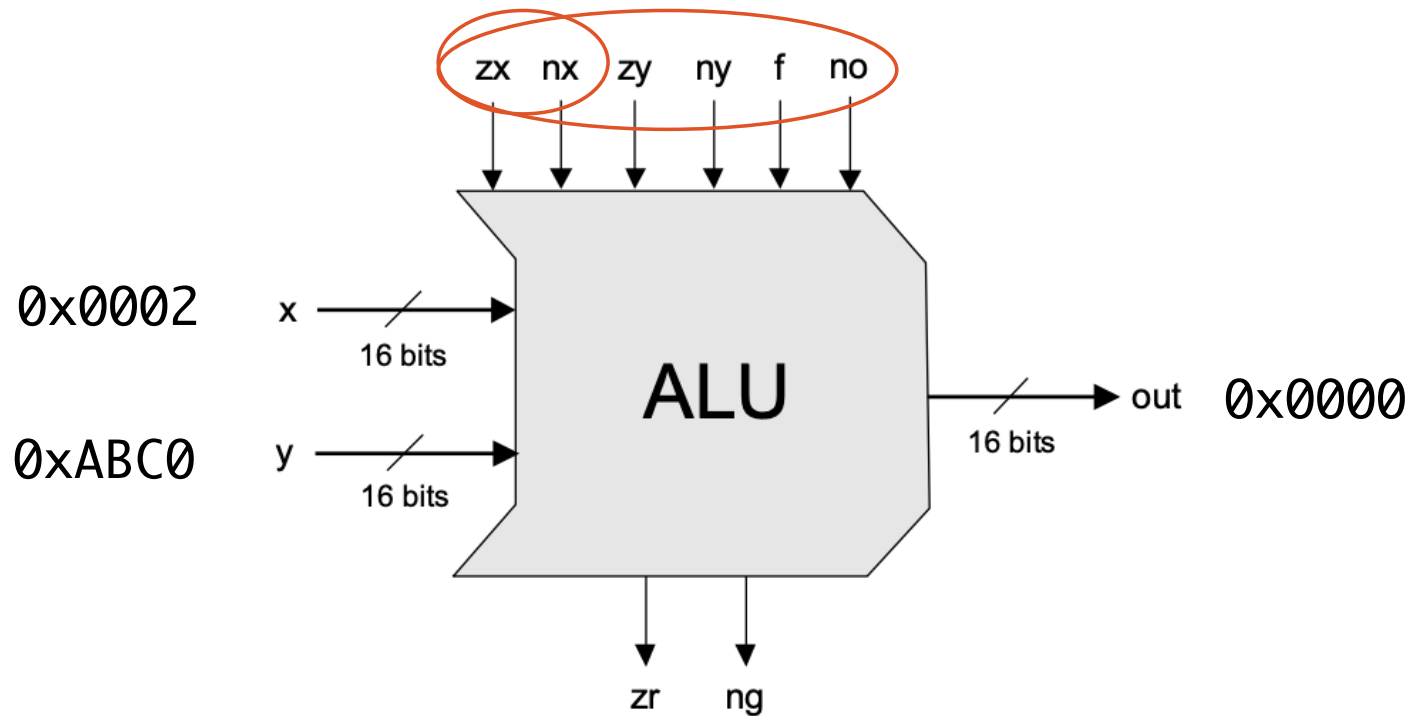


The Hack ALU operation

zx	nx	zy	ny	f	no	out
if zx then x=0	if nx then x=!x					

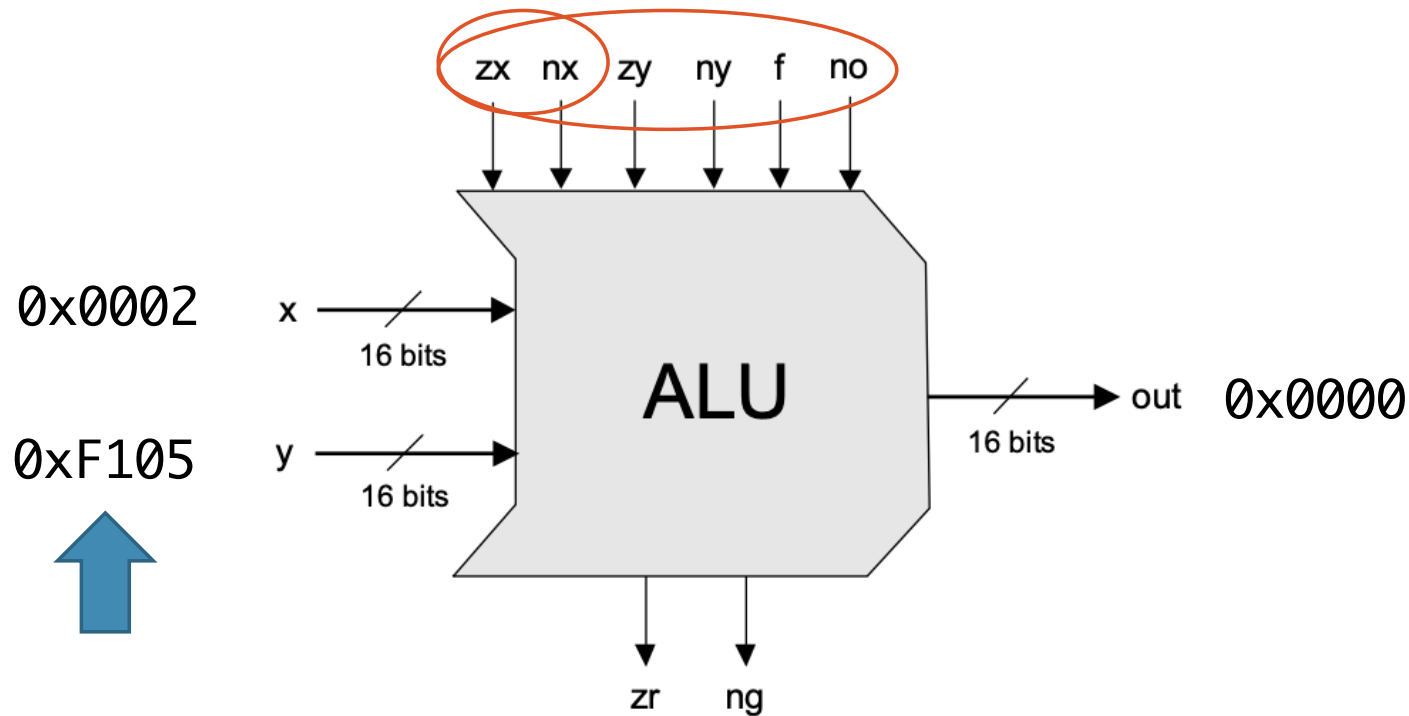

Hack ALU operation

pre-setting the x input		pre-setting the y input		selecting between computing + or &	post-setting the output	Resulting ALU output
zx	nx	zy	ny	f	no	out
if zx then x=0	if nx then x=!x	if zy then y=0	if ny then y=!y	if f then out=x+y else out=x&y	if no then out=!out	out(x,y)=

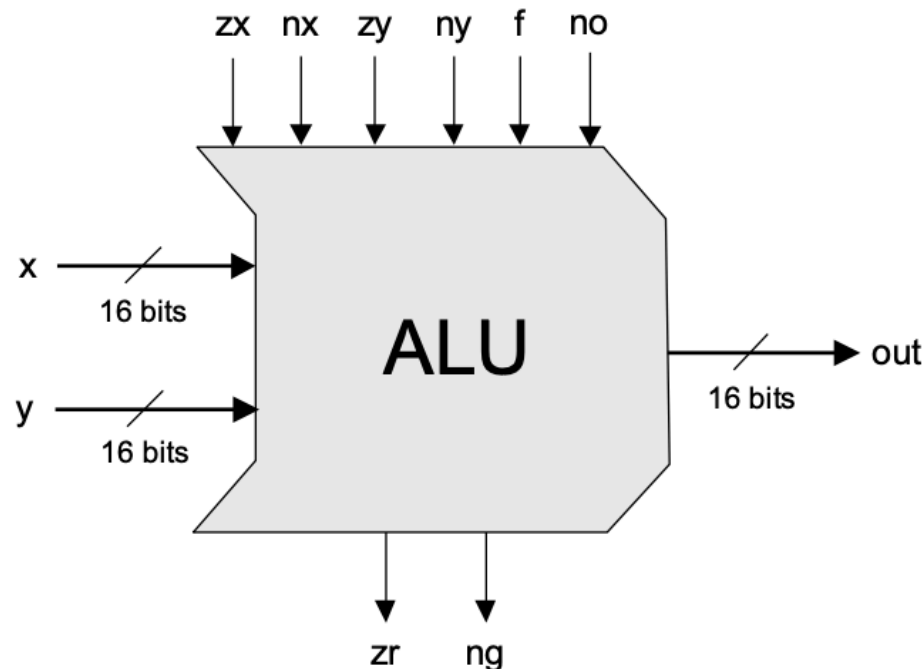

Hack ALU operation

- !x
- inverse x

pre-setting the x input		pre-setting the y input		selecting between computing + or &	post-setting the output	Resulting ALU output
zx	nx	zy	ny	f	no	out
if zx then x=0	if nx then x=!x	if zy then y=0	if ny then y=!y	if f then out=x+y else out=x&y	if no then out=!out	out(x,y)=
1	0	1	0	1	0	0
1	1	1	1	1	1	1
1	1	1	0	1	0	-1
0	0	1	1	0	0	x
1	1	0	0	0	0	y
0	0	1	1	0	1	!x
1	1	0	0	0	1	!y
0	0	1	1	1	1	-x
1	1	0	0	1	1	-y
0	1	1	1	1	1	x+1
1	1	0	1	1	1	y+1
0	0	1	1	1	0	x-1
1	1	0	0	1	0	y-1
0	0	0	0	1	0	x+y
0	1	0	0	1	1	x-y
0	0	0	1	1	1	y-x
0	0	0	0	0	0	x&y
0	1	0	1	0	1	x y

Example: compute !x

x:

y:

Following pre-setting:

x:

y:

Computation and post-setting:

Hack ALU

Example: compute y-x

x:

y:

Following pre-setting:


x:

y:

Computation and post-setting:

pre-setting the x input		pre-setting the y input		selecting between computing + or &	post-setting the output	Resulting ALU output
zx	nx	zy	ny	f	no	out
if zx then x=0	if nx then x=!x	if zy then y=0	if ny then y=!y	if f then out=x+y else out=x&y	if no then out=!out	out(x,y)=
1	0	1	0	1	0	0
1	1	1	1	1	1	1
1	1	1	0	1	0	-1
0	0	1	1	0	0	x
1	1	0	0	0	0	y
0	0	1	1	0	1	!x
1	1	0	0	0	1	!y
0	0	1	1	1	1	-x
1	1	0	0	1	1	-y
0	1	1	1	1	1	x+1
1	1	0	1	1	1	y+1
0	0	1	1	1	0	x-1
1	1	0	0	1	0	y-1
0	0	0	0	1	0	x+y
0	1	0	0	1	1	x-y
0	0	0	1	1	1	y-x
0	0	0	0	0	0	x&y
0	1	0	1	0	1	x y

Hack ALU output control bits

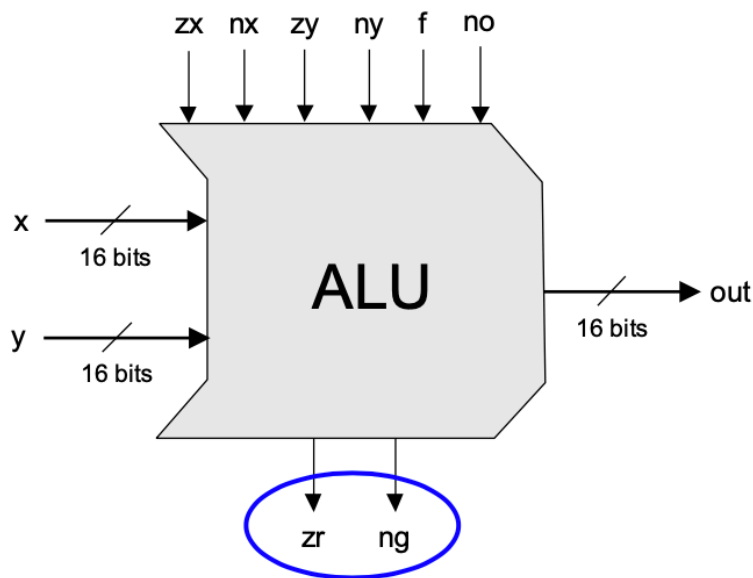

- if (out == 0) then zr = 1, else zr = 0
- if (out < 0) then ng = 1, else ng = 0
- ได้ใช้ zr และ ng เมื่อขั้นตอนการสร้าง
 - แยกคอมพิวเตอร์ ในบทที่ 4

Coming up: W2.5

Project

ภาพรวมโปรเจกต์ประจำสัปดาห์